

Lab Class 1
21.09.2021

- Frequency divider and counters.

Problems

1. Development of an 8-bit, 1 Hz counter with an 8-LED array display, working from 0 to 255.
2. Development of an 8-bit, 1 Hz counter with an 8-LED array display, working from 0 to 9.
3. Development of an 8-bit, 10 Hz counter with an 8-LED array display, working from 0 to 9.

Additional problems

1. Development of a 10 Hz counter, working from 0 to 99, with a 2-digits BCD coding and a 2 x 4-LED array display.
2. Development of a 10 Hz down counter.